

INDEX

A

- A - display, noise on : 15.2, 16.4
- A - scope, range measurement 18.2
- Acceleration : lag. 19.19
 - post-deflector, 6.24
- Acceptor : circuit 1.19
- Acorn valves : - see valves, acorn
- Active element : 1.2 (c)
- Addition and subtraction of vectors 1.10
- Addition, by long-tailed pair : 7.23
- Admiralty Handbook of Wireless Telegraphy : 1.1
- Admittance : characteristics : 4.6
 - characteristics of network 3.3
 - complex 1.11
 - generator 3.2
 - normalized 4.48
 - open-circuit, of network 3.3
 - short-circuit, of network 3.3
- Aerial : aperture of : 17.34, 17.48
 - arrays : 17.29, et seq
 - beacon : 17.30, 17.57
 - biconical horn : 17.57
 - cheese : 17.52
 - dielectric : 17.59
 - directional : 17.1, et seq.
 - effective area : 17.1
 - end-fed pair : 17.11
 - folded : 17.44
 - full-wave : 17.11
 - gain of : 17.1, et seq
 - gapless : 17.51
 - half-wave : 17.4, 17.10, 17.11, 17.12
 - centre-fed : 17.11, 17.12, 17.13, 17.35, 17.49
 - current-fed : 17.11, 17.12
 - end-fed : 17.11, 17.12, 17.13, 17.35
 - equivalent circuit : 17.12
 - Q of : 17.12, 17.13
 - voltage-fed : 17.11, 17.12
- Aerial : image 17.24, 17.32
 - input impedance of : 17.1, 17.11, 17.12, 17.13
 - long-wire : 17.59
 - microwave : 17.48 et seq
 - parasitic : 17.51, 17.42, 17.43
 - paraboloidal : 17.48
 - polyrod : 17.59
 - radiation resistance of : 17.11, 17.12, 17.13

INDEX

- receiving 17.14
 - effective cross-sectional area of : 17.15, 17.16, 17.17, 17.19
 - equivalent circuit of : 17.14
 - isotropic : 17.14, 17.15, 17.16, 17.17
 - matching of load to : 17.14
 - power gain of : 17.14, 17.15, 17.16, 17.17, 17.18
 - resonant length : 17.11, 17.12, 17.13
 - slotted : 17.55, 17.59
 - V-reflector : 17.59
 - Yagi : 17.42, 17.43
- Afterglow : 6.7
 - skiatron : 6.9
- Alternating current : regulator : 20.14
 - single phase transmission system : 19.7
 - stabilisation : 20.12
 - two-phase selsyn system : 19.8
- Alternating voltage regulator : 20.15, 20.16
- Ampere's rule : 4.3
- Amplidyne generator : 19.16
- Amplification : at centimetre wavelengths, disadvantages : 8.22
 - factor : 7.3
 - necessary for phase-shift oscillator : 8.20
 - of superregenerative circuit : 8.48
 - of valve : 7.3
 - of valve amplifier : 7.11
 - oscillators : 8.45
 - upper frequency limit of : 6.1
- Amplifier : equivalent circuit : see circuit
- Amplifiers : positive feedback : 8.3
 - valve : Ch.7
- Amplitude : and amplification, oscillators : 8.45
 - discrimination : 8.51
 - distortion : see distortion, amplitude.
- Amplitude : frequency characteristics : 16.3
 - modulated C.W. detection of : 12.1
 - of oscillation : 8.12
- Angle of flow : 7.4, 8.47
 - and signal voltage : 8.47
- Angular frequency, undamped natural : 19.19
- Anode : cathode ray tube : 6.4
 - current of cathode ray tube : 6.21
 - length of magnetron, effect of : 8.36
 - load, inductive, in feedback circuit : 7.16
 - modulation : 14.8
 - potential, effect on deionisation time : 6.38
 - power supply : 20.1
 - third - potential of : 6.27
 - transmitter : 6.33
 - voltage and deflection sensitivity : 6.16, 6.17
 - large for brilliance : 6.5
 - see power supplies, cathode ray tube
 - three-anode focusing : 6.12
 - two-anode focusing : 6.12
- Anomalous propagation : 17.28

INDEX

Antinodes : 4.13
Aperture, of aerial : 17.34, 17.48, 17.51
Applications of the circle diagram : 4.50, 4.53, 4.54
Arcs, complementary : 4.50
Area : effective cross-sectional, of receiving aerial : 17.15, 17.16, 17.17
 equivalent echoing of obstacle : 17.18
Array : broadside : 17.20 et seq
 end fire : 17.39, 17.40, 17.41, 17.43
 linear : 17.30, 17.37, 17.38, 17.55, 17.56, 17.57
 slotted : 17.55, 17.56
Artificial : inertia : 19.21
 viscosity : 19.21
Aspect of obstacle : 17.18
Assumption (servos) : 19.18
Astigmatism : see distortion, astigmatic
Attenuation : Coefficient in waveguides : 5.5
 constant, of filter sections : 3.10
 in waveguides : 5.23, 5.24
Attenuation : of network : 3.5
Attenuator : T - section : 3.7
 π - section : 3.7
 π - section in 2 - pole mixer : 16.19
 piston : 5.24
Automatic : bias 7.4. See bias
 frequency control : 8.49 - 8.54
 automatic sweep circuit : 8.53
 discriminator : 8.50 - 8.52
 effect on noise temperature ratio : 16.28
 mechanical : 8.49
 practical circuits : 8.54
 uni-directional pull-in : 8.54
gain control : 7.4, 16.37
 additional, for super-regenerative receivers : 8.48
 super-regenerative circuit : 8.48
potentiometer earthing circuit : 20.17
ranging unit 18.1

B

Back heating of cathode : 8.38
Balance - to - unbalance transformer : 4.38
Balanced : deflection - 6.18, 6.19, 6.20
 input - 6.30
 load : 4.38
 pair : 4.2
 pair (screened) : 4.38
Ballistic range correction : 18.4
Balun, quarter-wave : 4.38
Bandpass : circuits : 1.21
 coupling : 7.8
Bandwidth : 7.8
 aerial array : 17.45
 I.F. amplifier : 16.5, 16.6
 mirror aerials : 17.53
 optimum, of receiver : 16.4, 16.5
 RF amplifier : 6.3
 slotted array : 17.55

INDEX

Base : line stabilisation : 12.2
Batteries HT : 20.1
Bazooka : 17.49
Beam current : cathode ray tube : 6.3
Beam swinging : broadside array : 17.38
 with paraboloid : 17.50
 with slotted array : 17.55
Beam width : aerial array : 17.30, 17.36, 17.37, 17.39, 17.42
 paraboloidal aerial : 17.48
Beaming factor : aerial array : 17.30, 17.31, 17.32, 17.37, 17.39, 17.58
Bearing : in pentode, use in noise reduction : 15.9
Bends in waveguides : 5.46
Bias : for amplifiers : 7.4, 7.23
 for Class B or C operation : 7.4
 for pulse work : 7.4
 in soft CRT's : 6.14
Biasing circuits, oscillators : 8.46
Biconical horn : 17.57
Bifilar secondary impulse transformer : 14.7
Binomial : distribution of currents and aerial array : 17.37
 Coefficient : 4.35
Blacking-out, of cathode ray tube : 6.5, 6.31
Blocking oscillator : 10.8
Blocks, for magnetron : 8.37
Blowing, spark gaps : 6.40
Blumlein modulator : 14.39
Bombardment, positive ion : 6.37
Boltzmann's constant : 15.4, 15.7
Bootstrap premodulator : 14.21
Boundary layer capacitance, of crystal : 16.23
Breakdown time, soft rhumbatron : 6.42
Brewster : angle : 17.23, 17.24, 17.26
 effect : 17.23
Bridged : contact switching : 6.44
Brightening circuits, cathode ray tube : 6.31
Brilliance, CRT. 6.6, 6.12, 6.31
 current density : 6.6
 dependence on velocity of electrons : 6.6
Broad-band coverage : 4.35
 match 4.35
Broad-banking : 1.21
Broadside array : 17.23 et seq
Buffer stage : 8.2
Build-up : 4.40
Buncher, field distribution in : 8.22
Bunching : 8.22, 8.23
Bunching planes : 8.22
Burning of CRT screen focus : 6.14
Bypassing, to avoid paralysis : 16.38

C

Cables : disadvantage of, at cm. wavelengths : 5.5
Calibrators : 8.43
Can, quarter-wave : 4.38

INDEX

- Capacitance : 1.3
 - boundary layer, of crystal : 16.23
 - grid-cathode of pentode : 16.12
 - of diode mixer : 16.21, 16.26
 - inter-electrode : 7.7, 7.26, 8.3
 - " " variation in oscillators : 8.3
 - in parallel with feedback resistor for high-frequency responses : 7.16
 - inter-plate, of CRT : 6.30
 - self, in series IR circuit : 2.9
 - Stray : 7.9, 7.10, 7.23, 7.24, 7.26, 8.9
 - in push pull circuits : 8.19
 - Capacitive elements : 1.3
 - Capacitors : 1.3
 - Cartesian circle diagram : 4.49
 - Catcher : 8.22
 - Cathode : bias 7.4
 - bias, disadvantages of : 8.46
 - circuit, CRT : 6.31
 - emission density and transit time : 7.25
 - follower : 7.18, 7.19
 - Cathode : follower : 3.23, 16.36
 - for feeding deflector plates : 6.21
 - for large pulses : 7.18
 - regeneration in : 7.18
 - heating power : 20.1
 - input amplifier - see grounded-grid amplifier
 - inversion circuit : 7.23
 - lead inductance : 7.26 see also inductance, valve leads
 - ray tube : 6.1
 - ray tube : 6.3
 - glass envelope : 6.10
 - with extra anode ring : 6.24
 - size, radar transmitters : 6.33
 - structure, magnetron : 8.38
- Cavity : application of : 5.32
 - charges and currents on internal faces of : 5.29
 - excitation of : 5.30
 - field patterns in : 5.27
 - in cm. wave oscillators : 5.32
 - Q-factor of : 5.31
 - resonators : 5.25 et seq
- Centimetre : amplification, disadvantages of : 8.22
 - transmitters : 8.24
 - oscillations using triodes : 8.12, 8.16, 8.17
- Centimetric wave generators, principles of : 8.22
- Characteristics : admittance : 4.6
 - amplitude frequency : 7.8
 - diode, effect of gas : 6.35
 - impedance : 4.6
 - impedance of : 7.15
 - metrosil : 6.44
 - non-linearity of : 7.2
 - of amplifiers : 7.1
 - of CV 1065 : 6.34
 - of CV 1091 : 6.34
 - of load (servos) : 19.15
 - phase frequency : 7.8
 - suppressor grid - see suppressor grid characteristics

INDEX

- Characteristics : thermistor : 6.45
 - Thyratron : 6.38
 - video amplifier : 7.12
- Charge : density : 4.9
 - distribution : 4.3
 - of CRT bulb : 6.21
- Cheese : aerial 17.52 : 17.58
 - reflector : 17.52
- Choke : input filter (series) : 20.6
- Circle diagrams : 4.47
 - applications of : 4.50, 4.53, 4.54
 - cartesian : 4.49
 - examples : 4.50, 4.52 et seq
 - use of : 4.52
- Circular timebase : 11.12
- Circuit : amplitude discriminating : 8.51
 - equivalent, of Hartley and Colpitts oscillators : 8.8 - 8.9
 - " , of oscillators : 8.4 - 8.15
 - " , of valve amplifier : 7.3, 7.10, 7.15
 - for combined current and voltage feedback : 7.17
 - frequency stabilisation by resonance operation : 8.43
 - non-linear, and cathode follower : 7.19
- Clamping : 16.3, 16.37, 12.2
 - circuit : 7.4
 - switched circuits, : 12.3
- Class B operation : 7.4
 - C amplifier, similarity to VM tube, : 8.22
 - C operation, : 7.4, 8.3
- Clutter, sea : 17.26
- Coaxial line : 4.2
 - with spacing washers : 4.2
- Coefficient, binomial, 4.35
- Coils : 1.3
- Coil, ideal : 1.11
- Coincidence indicating system, : 19.12
- Cold block measurements, magnetron : 8.32
 - cathode diode : 6.36
- Colpitts oscillator : 8.9
- Common anode oscillator : 8.14
- Common cathode oscillator : 8.13
- Common grid oscillator : 8.15
 - T/R : 5.50
 - T/R circuits : 4.40
- Compensating inductance in video amplifiers : 7.11
 - thermistor : 6.45
- Complementary arcs : 4.50
- Complete standing wave : 4.13
- Complex admittance : 1.11
 - impedance : 1.11
 - numbers, use of : 1.8
 - quantities : 1.9
- Computing circuits, use of long-tailed pair : 7.23
 - devices 19.4
- Condensers : 1.3
 - ideal : 1.11
 - input filter (shunt) : 20.7

INDEX

- Conductance : 1.11
 - conversion : 16.17, 16.18
 - dynamics : 1.19
 - dynamic, of tuned circuit : 16.10 et seq
 - input due to cathode lead : 16.12
 - " due to transit-time : 15.10, 16.12
 - output of network : 3.3
 - transferred aerial : 16.10
 - transferred aerial, for minimum noise factor : 16.11, et seq
- Conduction angle : of linear diode mixer : 16.20
- Conductivity of ground : 17.20
 - of sea : 17.20
- Constant : amplification, by feedback 7.14
 - characteristic impedance line : 4.2
 - current generator : 1.4
 - current generator : 7.3
 - voltage generator : 1.4
 - voltage generator : 7.3
- Contactors coils, protection of : 6.44
- Contour diagrams, magnetron : 8.40
- Control grid, CRT : 6.5
 - ratio : 6.38
 - system : 19.1 et seq
- Conversion loss : of crystal mixer : 16.27, 16.29
 - of diode mixer : 16.26
 - of linear diode mixer : 16.20
 - of two-pole mixer : 16.19
- Converter-(see frequency converter)
- Cooling, anode : 6.33
- Copper oxide rectifiers : 20.2
- Corona, in triggered spark gaps : 6.40
- Coulomb, friction : 19.15
- Counter : 1.1
- Counting down multivibrator : 10.2
- Coupled circuits : 1.20
- Coverage broad-band : 4.35
- C - R circuit : application of instantaneous change of voltage to : 2.2
 - of linear voltage change to : 2.14
 - of rectangular voltage pulse to : 2.3, 2.5
 - of succession of rectangular voltage pulses to : 2.4
 - of succession of sawtooth pulses to : 2.16
 - of succession of triangular pulses to : 2.16
 - of trapezoidal pulse to : 2.15
 - of triangular pulse to : 2.15
 - use as differentiating circuit : 2.17
 - use as integrating circuit : 2.17
- C - R filter : 19.8
- CRT 6.1, 6.3, 6.10, 6.24
- Crystals, as filter elements : 3.14
 - capsule : 16.22
 - controlled oscillators : 8.18-see oscillators, crystal
 - equivalent circuit : 16.23
 - mixer : 16.22, 16.27
 - static characteristic : 16.22
 - valve : 16.22
- Cumulative grid detector - see detector, cumulative grid
- Current : and voltage feedback combined : 7.17
 - anode, of cathode ray tube : 6.21

INDEX

Current : extinction - see extinction current
feedback : 7.4, 7.14, 7.16, 7.22, 7.23
in spark gaps : 6.41
of deflector plate : 6.21
total, of cathode ray tubes : 6.27
Cut-off : 4.7
field, in magnetron : 8.25, 8.26, 8.34
frequency : 4.6
5.6, 5.10
of high-pass filter : 3.10
of low-pass filter : 3.10
wave-length : 5.6, 5.10
in septate guides : 5.21
of H O 1 wave : 5.11
Cylinder : cathode ray tube - see control grid : cathode ray tube
coaxial - as electron lens : 6.12
surrounding trigger electrode : 6.40

D

Damp, exclusion of : 6.44
Damping, by grid current : 8.45
critical : of L - C - R circuit : 2.10
factor : 18.19
of tuned circuit, effect on squegging : 8.47
parallel : 1.19
ratio : 1.21, 2.10, 19.19
Data : transmission systems : 19.1
transmissions systems (Non-Resetting) : 19.2
transmissions systems (Synchronous) : 19.2
Datuning 18.4
DC restoration : 2.4, 12.2
Diaphragm
Aparative 5.43
inductive 5.43
in circular waveguides 5.43
resonant 5.43
, Q-factor 5.43
Dead zone : 19.16
Decoupling : 7.6
of screen to cathode : 7.16
Decrement, logarithmic : 2.10
Definition (servos) : 19.18
Deflection, balanced : 6.18, 6.19, 6.30
defocusing - see defocusing deflection
direction of in double-beam tube : 6.25
Deflection.: electric : 6.16, 6.28
magnetic : 6.17, 6.29
sensitivity : 6.16, 6.17
and focus : 6.16
and distortion : 6.18
Deflector : plates, corrected for distortion : 6.18
plate current : 6.21
plate current : 7.19
plates, input circuit to : 7.30
post-deflector acceleration : 6.24
sensitivity, high : 6.24

INDEX

- Deflection : systems, comparison : 6.33
- Defocusing, deflection : 6.19
- Deionisation : 6.38, 6.39
- Delay : in building-up bias : 8.47
 - line, design of : 3.16
 - line, production of rectangular pulses by : 3.16
 - locking 18.4
- Delay network : advantages of : 14.27
 - application of instantaneous change of voltage to : 2.11
 - charging from an AC voltage source : 14.27
 - charging from steady voltage source : 14.23
 - choke charging : 14.23
 - constant-current charging 14.24
 - delay time : 2.11, 3.16
 - line : 3.15, 3.16
 - rigging in : 3.11
 - symmetrical charging : 14.25
- Delay : of start of transmitter pulse : 8.34
 - time, of RF amplifier : 16.3
- Derivative : error control: Use of : 19.21
- Detector : 16.5, 16.30
- Detection : 12.1
- Dielectric: aerial: 17.52
 - constant : 4.7
 - constant of atmosphere : 17.28
 - lenses : 17.52
 - losses : 4.41, 4.42
 - rod : 4.2
- Differential output resistance : 20.9
 - receiver : 19.12
 - resistance - see resistance, differential
- Differentiating circuit : 7.10
- Differentiation, by CR circuit : 2.17
- Diffraction, of radio waves round earth : 17.28
- Diode : as mixer, 16.20, 16.26
 - characteristic - see characteristic
 - cold cathode : 6.36
 - equivalent, of triode : 15.8
 - half-wave rectifier : 20.3
 - hot cathode : 6.37 (see mercury vapour rectifier)
 - limiting circuits : 9.2
 - slope conductance : 15.7
 - space charge limited, noise in : 15.16
 - space charge in - see space charge
 - temperature limited, noise in : 15.6
- Direct current : generators 20.1
 - motors : 19.16
 - restoration : 2.4, 12.2
- Direct wave : 4.8
- Direction of voltage, spark gap : 6.40
- Director, parasitic : 17.41, 17.42
- Discharge : of open circuited line : 4.12
 - valve : 4.40
- Discriminator : 8.50, 8.52
- Displacement correction, for range : 18.4
- Display : 6.1
- Display, A-type, noise on : 15.2, 15.16
 - A-type, temporal gain on : 16.40
 - PFI noise on : 15.16
 - PFI temporal gain on : 16.40

INDEX

Distortion : amplitude : 7.2, 7.9, 7.14
and negative feedback : 7.14
astigmatic : 6.20, 6.23, 6.28, 7.23
avoidance by cathode follower : 7.19
by transformer : 7.15
Distortion : cathode ray tube : 6.18 - 6.22
deflector plate current : 6.21
defocusing : 6.19, 6.28
frequency : 7.2, 7.9
grid, current : 7.4
in detector : 16.5
in paraphase amplifiers : 7.22, 7.23
of amplifiers : 7.2
of pulse by delay line : 3.15
of rectangular pulse by C-R circuit : 2.3
of RF pulse in receiver : 16.1, 16.3
phase : 7.2, 7.9
stray field : 6.22
trapezium : 6.18, 6.28
unbalanced, in phase splitter : 7.22
with sideback : 7.4
Distortionless line : 4.6
Distrene : 4.45
Distributed : constants : 4.1
elements : 4.17, 4.18
Distribution : instantaneous : 4.5
Disturbances : evanescent : 4.7
Doorknob valves - see valves, doorknob.
Double-beam tube : 6.25
Double - decoupling : 7.6
quarter-wave line : 4.35
quarter-wave transformer : 4.54
shunt stub : 4.54
stream steady state : 8.28
tuning plunger : 5.47
Drift space : 8.22
Drift space entry velocity : 8.22
Driver, aerial : 17.41
Duplicate systems : 19.2
Dust core : 7.8
Dynamic : conductance : 1.19
errors : 19.3
resistance : 1.19
resistance : 7.8
of resonant lines 7.26
Dynatron : 8.10
Dynatron mode : 8.24, 8.26

E

Earth's magnetic field, effect on cathode ray tube : 6.22
Earthing, in oscillator circuits : 8.16
Eccles-Jordan circuit : 10.1
Echelon strapping : 8.35

INDEX

- Echo boxes
- Echoing area : equivalent, of obstacles : 17.18
 - of flat metal plate : 17.18
 - of medium bomber : 17.18
- Efficiency : 8.3
- Efficiency of magnetrons : 8.35, 8.40
- Electric fields : 4.1
- Electrode, keep-alive : 4.40
- Electromagnetic field : 17.2 et seq
- Electromagnetic induction, Faraday's Law of : 1.3, 4.1
 - energy density in : 17.6, 17.7
 - power relations : 17.7
 - propagation
- Electrode, starter : 6.42
 - wear in spark gaps : 6.40, 6.41
- Electrometer, analogy with magnetron : 6.30
- Electron : flow in magnetic field : 6.13
 - in electrostatic field : 6.16, 8.25
 - in magnetic field : 6.17, 8.25
 - lens, simple : 6.12, 6.28
 - lens, compound : 6.12, 6.18
 - optics : 6.12
 - orbits in magnetrons : 8.25, 8.26
 - radial velocity : 6.13
- Electron spiral : 6.13
- Electron spiral : 6.13
- Electronic devices : Ch.6
 - potentiometer earthing circuit 20.17
- Electrons, secondary, from cathode ray tube screen : 6.21
- Electrostatic focusing - see focusing electrostatic
- Element : active 1.2 (c) 1.4
 - capacitive : 1.3
 - inductive : 1.2 (b), 1.3
 - resistive : 1.3
- Elements : distributed : 4.17, 4.18
 - linear : 1.3
- Elliptical timebase : 11.12
- Energy : density, in electromagnetic wave : 17.12
 - losses : 4.25
 - of the wave : 4.8
 - transfer criterion and potential : 8.32
- End-plate distance : 8.36
- Equipotential : lines, curved : 6.18
 - planes and refractive index : 6.12
 - surfaces, and trapezium distortion : 6.18
- Equivalent : circuit, for noise in first stage : 16.10 et seq
 - for two pole mixer : 16.19
 - of cathode follower : 7.18
 - of half wave aerial : 17.12
 - of magnetron : 8.27
 - of Hartley's and Colpitt's oscillator : 8.4 to 8.15
 - circuits : oscillators : 8.4, 8.15
- Equivalent network : 1.3
- Equivalent series and parallel networks : 1.17
- Error control, simple : 18.19
- Error control, simple : limitations of : 19.20
 - simple, use of derivative and integrated : 19.21
 - steady state (servos) : 19.19

INDEX

Evanescent attenuation of : 5.24
Evanescent disturbance : 4.7
 modes : 4.7
 modes in waveguides : 5.12
E-vectors : 4.3
E waves in circular guides : 5.19
 in rectangular guides : 5.6 et seq
Exponential wave : 4.5
Extinction current : 6.36
 voltage : 6.36, 6.37, 6.38, 6.42

F

Faraday's Law of electromagnetic induction : 1.3, 4.1
Feed : primary : 17.49, 17.52, 17.53
 tapered : 17.37
Feedback : 7.14, see negative feedback
 at high frequencies : 7.26
 at low frequencies only : 7.17
 combined I & V : 7.17
 constant : 7.15
 constant amplification by : 7.14
 equivalent circuit : 7.15, 7.16
 in klystrons : 8.22
 negative, reduction of short noise by : 15.9, 15.15, 16.12, 16.14
 parallel : 7.14, 7.15, 7.22
 positive : 8.3
 voltage : 7.14, 7.15, 7.22
Feeding, of broadside array : 17.35, 17.37
 of paraboloid : 17.49, 17.53
Field discharge resistor : 6.44
Field, electric : 4.1
Fields: induction : 4.6
 magnetic : 4.1
 storage : 4.7
 stray : 6.22
Field strength : diagram of aeriels : 17.13, et seq
 of earth : 17.24, 17.25, 17.26, 17.46, 17.47, 17.58
 of obstacle : 17.18
 factor : 17.4, 17.26
Filter : ACW : 3.14
 band-pass : 3.13
 band-stop : 3.13
 high-pass : 3.9, 3.10, 3.13
 ideal : 3.8
 in detector circuit : 16.5
 low-pass : 3.9, 3.10, 3.11, 3.12, 3.16
 low-pass : 1.21
 m-derived : 3.14
 prototype : 3.9
First order servo, speed control : 19.22
Fleming, William : 10.6
Floating paraphase amplifier : 7.23
Fluorescent screen : 6.7
Flyback, elimination of : 6.31

INDEX

- Focus : and deflection sensitivity : 6.16
 - and speed of electrons : 6.19
 - deterioration with long tube : 6.17
 - of CRT : 6.12
 - of dependence on brilliance : 6.14
- Focusing : electrostatic : 6.12
 - gas : 6.14
 - inertia in : 6.14
 - magnetostatic : 6.13, 6.23
 - system, cathode ray tube : 6.4, 6.11
 - three-anode : 6.12
 - two-anode : 6.12
 - comparison : 6.23
- Folded half-wave aerial : 17.44
- Follow-up time : 18.2
- Foster-Seeley type discriminators : 8.52
- Fourier analysis : 7.1
 - analysis of double input mixer : 16.18
 - of rectangular pulses : 16.2
 - of two poled converter : 16.19
- Frequency : characteristics of RF amplifier : 16.3
 - characteristics of two-terminal networks : 1.18
 - of video stages : 16.5, 16.6
 - converter : 16.5, 16.15, 16.16
 - crystal : 16.15
 - diode : 16.15, 16.20, 16.24, 16.25
 - hexode : 16.15, 16.16, 16.24, 16.25
 - noise in : 16.24, 16.25
 - pentode : 16.15, 16.16, 16.17, 16.24, 16.25
 - triode : 16.15, 16.16
 - two-pole : 16.16, 16.19
 - two-pole : analysis : 16.19
 - cut-off, of delay liner : 3.15
 - of filter sections : 3.10, 3.1, 3.12, 3.13, 3.14
- Frequency : discrimination by feedback : 7.15
 - distortion - see distortion frequency
 - divider multivibrator : 10.2
 - effects : 4.44
 - effect of magnetron current on : 8.41
 - natural angular undamped : 19.19
 - natural undamped : 19.19
 - of infinite attenuation of filter section : 3.14
 - of magnetostriction oscillator : 8.7
 - of RF amplifier : 16.3
 - pulling : 8.40, 8.41
 - range, at centimetre wavelengths : 8.23
 - resonant : 1.18
 - response, control system : 19.3
 - separation of modes, by strapping : 8.35
 - spectrum and video amplifiers : 7.12
 - splitting : 8.41
 - spread : 8.1
 - stabilisation : 8.43
 - stability, magnetrons : 8.40
- Friction : coulomb : 19.15
 - static : 19.15
 - viscous : 19.15
- Full wave : rectifier 20.3
 - rectifier bridge : 20.3
 - rectifier, three-phase : 20.4

INDEX

G

- Gain control : automatic : 16.37
 - valve : 16.36
- Gain control manual : 16.36, 16.38
 - of IF amplifier : 16.35
 - of network : 3.5
 - power of aerial : see power gain
 - swept : 16.40
 - temporal : 16.40
- Gap, filling : 17.27, 17.47
 - in radar coverage : 17.2b
 - spark : 4.4c
- Gapless aerial : 17.51
- Gas discharge : 4.40
 - in valves 6.35
- Gate pulse : 16.37
 - valve : 16.37
 - valves : 6.34
- Gating circuit, for AGC : 16.37
- Gaussian distribution : 17.37, 17.48
- Generator, constant current : 1.4
 - constant voltage : 1.4
- Geometrical discontinuity : 4.7
- Glass envelope, CRT : 6.10
- Glow discharge, in rhumbatron : 6.42
- Goniometer : 3.20, 3.21, 18.3
- Grating factor : 17.30
- Grid : bias, in soft cathode ray tubes : 6.14
 - circuit, cathode ray tube : 6.31
 - coupling condensers : 7.19
 - current, analogy with deflector current : 6.21
 - and cathode followers : 7.18, 7.19
 - avoidance of use of
 - limiting action in oscillators : 8.45
 - thyatron : 6.38
 - disadvantage of : 14.7
 - effect of, in thyratrons : 6.38
 - leak, for oscillator bias : 8.46
 - leak returned to high potential : 8.47
 - modulation : 14.3
- Ground electrical properties of : 17.20
 - reflection of radio waves by : 17.20, 17.21, 17.23, 17.46, 17.47, 17.58
- Grounded grid amplifier : 7.20
- Group velocity : 5.6

H

- Half-wave loop : 4.38
 - rectifier : 19.3
 - rectifier, three-phase : 20.4
- Hard valve : 6.32, 6.34
 - stabilisers : 20.12
- Harmonic response (servos) : 19.19
- Harmonics, avoidance of : 8.19
 - in Colpitt's oscillator : 8.9
 - production of : 6.44, 8.8, 8.19

INDEX

Hartley oscillator : 8.8
Head amplifier : 16.34
Heater windings, insulation of : 7.16
Heating power, cathode : 20.1
Heil tube, 8.23
Helmholtz's Theorem : 1.12
High-capacitance loads, feeding of : 7.19
High gain, of superregenerative receivers : 8.48
High power from oscillators : 8.16
High Q rejector circuits : 8.51
High tension batteries : 20.1
 supply - see power supplies
Hole and slot magnetions: 8.27
Horn, biconical : 17.57
Hot cathode mercury vapour rectifiers : 20.2
Hunting : 19.16
H-vectors : 4.3
Hoz wave : 5.9
H waves in circular guides : 5.19
H waves in rectangular guides : 5.6

I

Ideal coil : 1.11
Ideal condenser : 1.11
Illumination of aperture : 17.48
 of targets : 17.51
Image, aerial : 17.24, 17.32
Impedance, characteristics : 4.6
 of attenuator : 3.6
 of filter : 3.10, 3.11, 3.12, 3.13
 of network : 3.3
 complex : 1.11
 conjugate : 3.4
 input, of aerial : 17.1, 17.11, 17.12, 17.13
 input, of network, 3.1, 3.2
 input of 2-pole mixer : 16.9
 input, of valve, due to cathode lead : 16.12
Impedance, magnitude of : 1.11
 normalised 4.48
 open-circuit : 3.3
 output : 1.12
 output, I.F., of crystal in mixer : 16.27
 output, of network : 3.1, 3.2
 output, of 2 pole mixer : 16.19
 purely reaction : 1.11
 radiation, of aerial : 17.41, 17.44
 short-circuit : 3.3
 single : 4.6
 source, of network : 3.1
 transformers : 4.34
 transforming devices : 4.2
 wave, of free space : 17.7
 improperly terminated : 4.5
Indicating systems, coincidence : 19.12
Inductance : 1.3
 cathode lead, damping due to : 16.12
 grid lead : 16.13
 lead, of diode mixer : 26.21
 of valve leads : 7.24, 7.26, 8.19, 8.43
 screen lead : 16.13

INDEX

- Inductors, mutual : 1.3
 - self : 1.3
- Induction fields : 4.66
 - motors, two-phase : 19.16
- Inductive elements : 1.3
 - potentiometers : 18.6
 - wire in a waveguide : 5.43
- Inertia, artificial : 19.21
- Infinite line : 4.5
- Input admittance : 7.7
 - balanced : 6.30
 - capacitance : 7.7, 7.25
- Input capacitance, cathode follower : 7.18
 - circuit, blackout : 6.31
 - circuits, cathode ray tube : 6.30, 6.31
 - conductance, cathode-follower : 7.18, 7.26
 - damping : 7.26
 - deflector plates : 6.30
 - impedance and transit time : 7.25
 - impedance, of cathode ray tube : 6.30
 - impedance of loss-free line : 4.16
- Instability, of RF discharge : 6.42
- Instantaneous distribution : 4.5
- Insulators, metallic : 4.29, 4.54
- Integrated error control, use of : 19.21
- Integration, by CR circuit : 2.17
- Intensity modulation : 6.1
- Interaction, of electric fields : 6.18
- Interference : 4.4
 - adjacent channel : 16.5
 - factor, of aerial : 17.24, 17.46, 17.58
 - from oscillators, reduction of : 8.19
 - lobes : 17.24, 17.46
 - second channel : 16.5
- intermediate-frequency amplifier, gain of : 16.35
 - choice of : 16.5
- Ionisation - see deionisation
 - by control electrode : 6.39, 6.40
 - by light : 6.40
- Ionisation : in soft valves : 6.35, 6.37, 6.38
 - potential : 6.35, 6.40
 - residual : 6.40
 - rhumbatron : 6.42
- Ions, in soft cathode ray tube : 6.14
- Iris : 5.45
 - matching : 17.35
 - reflecting : 5.45
 - rotating : 5.45
- Isotropic radiator, : 17.5, 17.8, 17.9, 17.18, 17.24, 17.26, 17.31
 - 17.34, 17.39, 17.46, 17.47, 17.58
- Inverse square law : 17.2

J

- J-scope timebase : 18.20
- Jitter : 6.40
 - in rotary spark : 6.41
 - in triggered spark : 6.40

INDEX

Joint : rotating : 4.30
sliding : 4.36
Joints in waveguides : 5.46

K

Keep-alive electrode : 6.42, 6.40
'Killers' for cathode ray-tube screen : 6.7
Kirchoff : 1.2, 4.1
Klystron : 8.23
double rhumbatron : 8.23
Klystron, as local oscillator : 16.28
noise in 16.28

L

Lamp transmission system : 19.4 (i)
Launching waves in guides : 5.14, 5.22
LCR circuit application of instantaneous change of voltage to : 2.10
free oscillations in : 2.10
in diode mixer : 16.21
Lead inductance - see inductance of valve leads
Lecher bars : 4.28
Lenses, dielectric : 17.52
Life, of spark gaps : 6.40, 6.41
Light, ionisation by : 6.40
Lighthouse tube circuit : 8.16
Lightning arrester : 6.44
Limitation, of pulse : 16.3
Limitations of simple error control : 19.20
of transmission lines : 4.41
Limiter : 7.4
Limiting circuits : diode 5.2
triode and pentode : 5.3
resistor, in mercury - vapour rectifier : 6.37
in thyatron anode : 6.38
in thyatron grid : 6.38
Line, artificial : 3.6, 3.15, 3.16
Line characteristics : 4.11
distortionless : 4.6
double quarter-wave : 4.35
fed by DC generator : 4.10
infinite : 4.5
quarter-wavelength : 4.27
unbalanced : 4.38
Linear circuits : 1.3
control system : 19.2
elements : 1.3
networks : 1.3
Linearity of potentiometer : 7.19
Lines, as tuned circuits : 7.8
non-resonant : 4.26
resonant : 4.26

INDEX

Load, balanced : 4.38
 characteristics (servos) : 19.15
 resistance : 4.8
 variations - effect on magnetron : 8.41
Loading, of oscillators : 8.2
Long afterglow - see afterglow
Long lines, effect on frequency : 8.41
Long tailed pair - see cathode inversion circuit
Loop, half-wave : 4.38
LR circuit, application of instantaneous change of voltage to : 2.6
 application of rectangular voltage pulse to : 2.7
 application of succession of rectangular voltage pulses to : 2.8
 disadvantages of, compared to series C.R circuit : 2.9
 response to series of sawtooth pulses : 2.16
 response to series of triangular pulses : 2.16
Loss : coefficient in waveguides : 5.23
 conversion of crystal : 16.27, 16.29
 of diode mixer : 16.26
 of two-pole mixer : 17.19
Loss-free line, input impedance : 4.16
 transmission line : 4.3
Loss : insertion of filter sections : 3.11, 3.12, 3.13, 3.14
Loss : of energy : 4.2
 of network : 3.5
Losses, dielectric : 4.41, 4.43
 in open wire feeder : 4.46
 resistive : 4.41, 4.42
Lossy line : 4.18
Low-frequency feedback : 7.15
 pass filter : 1.21
Lumped constants : 4.1

M

Magaw split-anode magnetron : 8.24
Magnetic : deflection and current feedback : 7.16
 and trapezium distortion : 6.18
 non-uniform field : 6.18
 field : 4.1
 field, out-off value : 8.25 - see out-off field
 field of earth, effect on cathode ray tube : 6.22
 permeability : 4.7
Magnetostatic focusing - see focusing, magnetostatic
Magnetostriction oscillator : 8.7
Magnetron : analogy with electrometer : 8.30
 anode length : 8.36
 block : 8.27
 built-in matching device : 8.40
 cavities, direction of field : 8.32
 cold block measurements : 8.32
 contour and Rieke diagrams : 8.40
 distribution of anode voltage and charge : 8.32
 end plate distance : 8.36
 energy supply criterion : 8.33
 heater supply : 8.38
 initiation of oscillation : 8.32
 internal construction : 8.25
 modes of oscillation : 8.31
 operating conditions for : 8.34
 output loops : 8.37
 preplumbed : 8.42
 pretuning : 8.35

INDEX

Magnetron : rising sun : 8.27
split anode : 8.24, 8.26
standing and travelling waves : 8.31
stub tuner close to, 8.41
tunable : 8.36
two segment : 8.24, 8.26
unstrapped, operating condition : 8.34
wavelength : 8.36
Magnetrons : 8.24 - 8.42
Magslip : 3.17, 3.19
Magslip receiver : 19.11
Marx circuit : 14.38
Master oscillators : 8.43
oscillator and power amplifier combined : 8.43
Match broad-band : 4.35
Matching : 4.32
Matching : 4.32
by iron-cored transformer : 3.4
by slugs : 4.54
by stubs : 4.36
device diaphragms : 5.43
double stud : 4.36, 4.54
of aerial to load : 17.14
of aerial to transmission line : 17.44
of crystal in mixer : 16.22, 16.27
of network and load : 5.4
sections : 4.32
sections, quarter wave : 4.34
sections, trombone : 4.38
wide band : 4.38
Medium, unbounded : 4.7
Meissner oscillator : 8.6
Mercury arc rectifiers : 20.2
Mercury : light, for skiatron : 6.9
vapour rectifier : 6.37
vapour rectifiers : hot cathode : 20.2
Mesh : 1.2
Metadyne system : 19.16
Metallic insulators : 4.29, 4.54
Metrosil : 6.44
Microwave oscillators : 4.46
Miller effect : 7.7, 7.10, 7.18, 7.20, 7.22
Miller timebase : 11.10
principal circuits employing : 10.9
Mirror sheese : 17.52, 17.58
cosec 20 : 17.51
paraboloidal : 17.48 et seq
special shapes of : 17.51
used with slotted array : 17.56
Mismatch : 4.24

INDEX

- Mixer : 16.15
 - balanced : 16.28
 - coaxial : 16.22
 - crystal : 16.22, 16.27, et seq
 - diode, bias resistor : 16.26
 - linear, analysis of : 16.20
 - noise in : 16.26
 - non-linear : 16.20
 - double input, analysis of : 16.17
 - class A operation of : 16.18
 - class C operation of : 16.18
 - hexode : 16.18, 16.24, 16.25
 - pentode : 16.17, 16.24, 16.25
 - single input, analysis of : 16.17
 - disadvantages of : 16.17
 - triode : 16.17, 16.24, 16.25
 - two-pole, analysis of : 16.19
 - equivalent circuit of : 16.19
 - waveguide : 16.22
- Mixing, orders of 16.16
 - variation of efficiency with : 16.16, 16.18
- Mode number : 8.31
- Modes : 4.7
- Modes, of magnetron : 8.31
 - principal : 4.7
- Modes : supplementary : 4.7
- Modulation : anode : 14.8
 - anode self-quenching : 14.6
 - by transit time of guide : 8.41
 - cathode follower : 14.4
 - delay network : 14.11
 - depth, in VM tube : 8.22
 - disadvantage of : 14.7
 - envelope, superregenerative receiver : 8.48
 - grid : 14.3
 - grid self-quenching : 14.5
 - hand valve method : 14.9
 - pulse, of transmitters : 14.
- Modulators : 6.39
- Motors : DC : 19.16
 - servo : 19.16
 - two-phase induction : 19.16
- Multiple layer screens, for CRT : 6.8
- Multiplying voltage circuits : 14.37
- Multivibrator : 10.12
 - cathode-coupled : 10.3
 - counting-down : 10.2
 - electron-coupled : 10.4
 - frequency of : 10.2
 - synchronisation of : 10.2
 - with grid leaks connected to HT. : 10.2
- Mumetal shield : 6.22
- Mutual conductance : 7.3
 - of CV1091 and CV1065 : 7.8
- Mutual inductance : 8.4

INDEX

N

- N-arcs : 4.49
- Natural angular frequency, undamped : 19.19
- Natural frequency, undamped : 19.19
- Negative conductance : 7.7
 - feedback : 7.14, 7.20, see also feedback and generator output impedance : 7.17
 - in paraphase amplifiers : 7.22, 7.23
- Negative resistance : 8.3, 8.10, 8.26
 - viscosity : 19.21
- Neon : limitations of : 6.36
 - valves : n : 6.36
 - valve stabilisers : 20.10
- Network : balance : 3.1
 - delay : 3.15
 - delta : 1.13
 - equivalent : 1.3
 - four-terminal : 3.1
 - iterative : 3.1, 3.6
 - linear : 1.3
 - parallel : 1.15
 - phase-shifting : 3.23, 3.24
 - resolving : 3.17
 - series : 1.14
 - star : 1.13
 - symmetrical : 3.1, 3.3
 - T-section : 3.1, 3.3, 3.6
 - π - section : 3.1, 3.3, 3.6
 - unbalanced : 3.1
- Neutralisation of triode : 7.7
- Nitrogen peroxide, in sparks : 6.40
- Nodes : 4.13
- Noise : aerial : 15.4, 15.10, et seq, 16.27
 - atmospheric : 15.1
 - avoidable : 15.1
 - carbon resistor : 15.11
 - circuit : 15.3
 - cosmic : 15.1
 - factor : definition of : 16.9
 - effect of signal frequency on : 16.32
 - of crystal mixer : 16.27, 17.29
 - of diode mixer : 16.26
 - of grounded-grid triode, first stage : 16.14
 - of pentode, first stage : 16.12, 16.13
 - of receiver : 16.10, et seq
 - flicker, 15.11
 - high-frequency : 15.10
 - induced grid 15.3, 15.9, 16.12, 16.13, 16.25, 16.26
 - infrequency converters, 16.24, 16.25, 16.26, et seq
 - in klystron amplifiers 8.22
 - in receiver, general, 16.1 et seq.
 - in superregenerative receivers : 8.48
 - ionisation : 15.11
 - Johnson : 15.3
 - local oscillator 16.27, 16.28
 - "man-made" : 15.1
 - of tuned circuit : 15.4
 - partition : 15.3, 15.9, 16.12, 16.13, 16.25, 16.26
 - reduction of 16.13

INDEX

Noise : resistance equivalent of hexode : 16.25
of pentode : 15.14, 16.25
of triode : 15.12, 15.13, 16.25
secondary emission : 15.11
shot : 15.3, 15.5, 16.12, 16.13, 16.25, 16.26, 16.28
shot in diode : 15.6, 15.7, 16.26
in klystron : 16.28
in pentode : 15.9
in triode : 15.8
sources: equivalent circuits of : 15.4
temperature ratio : effect of AFC on : 16.28
temperature ratio : of crystal : 16.27, 16.28
effect of crystal current on : 16.27
effect of IF on : 16.29
Non-linear circuits : 1.5
and cathode follower : 7.19
Non-ohmic circuits : 1.5
Non-resonant lines : 4.20
Non-uniform field, for focusing : 6.13
Normalised admittance : 4.48
Normalised impedance : 4.48
Norton's Theorem : 1.12



Ohm's law : 1.3, 4.1
Open-wire feeder, losses in : 4.46
Open-wire line : 4.2
Orbits, shape of, in magnetrons : 8.25
Oscillation, maintenance of : 8.3
maintenance of in magnetron : 8.26
Oscillations, free, of LCR circuit : 2.10
Oscillator, amplitude control for : 8.20
effect of transit time : 7.25
Oscillators : analysis of working of : 8.44
anode self-quenching : 8.47
biasing for : 7.4
Colpitt's : - 8.9
common anode : 8.14
common cathode : 8.13
common grid : 8.15
control of oscillation amplitude : 8.12
crystal : 8.18
disadvantage of common cathode circuit : 8.12
Hartley : 8.8
Meissner : 8.6
microwave : 4.46
non-self starting : 8.45
practical details : 8.17
push-pull : 8.19
resistance capacitance : 8.20
self-quenching : 8.47
squegging : 8.47
triode, at 600-3000 Mc/s : 8.12, 8.16, 8.17
tuned-anode : 7.7, 8.12, 8.5
tuned-grid : 8.4, 8.12
velocity modulated : 8.21, 8.22, 8.23
Wien bridge : 8.20

INDEX

Oscillators : with class C bias : 8.45
with two tuned circuits : 8.12
Output loop : 8.37
impedance : 1.12
impedance, cathode follower : 7.18
impedance with current feedback : 7.16
resistance of valve : 7.3
Overswing diode : 14.16
Oxygen for deionisation : 6.40

P

Paraphase amplifiers : 7.21, 7.22, 7.23
Parallel damping : 1.19
feedback : 7.14, 7.15, 7.22
networks : 1.15
pair : 4.2
Paralysis cathode : 16.38
grid : 16.38
Paraboloidal mirror : 17.48 et seq
Parasitic aerials : 17.41 et seq
Partial standing wave : 4.13
Passive element : 1.2(b) : 1.3
Pawsey stub : 4.38
Pentode, acting as tetrode : 6.34
as video-amplifier : 7.13
low-noise : 16.13
upper frequency limit of : 16.13
Performance : of servo systems : 19.17
of transmission systems : 19.3
Permeability : Magnetic : 4.7
tuning : 7.8
Phanastron : 10.11
Phase : angle : in crystal oscillator : 8.18
in double-tuned circuit oscillator : 8.12, 8.13
in resistance - capacity oscillators : 8.20
centre of aerial : 17.4, 17.24, 17.26, 17.30, 17.31, 17.37, 17.46, 17.48, 17.49
characteristic of RF amplifier : 16.3
delay : 1.21
discrimination : 8.52
distortion : 7.2, 7.9
Phase : frequency relation : thermistors : 6.45
goniometer : 18.3
measurement : 18.3
of feedback voltage : 7.14
of reflection, effect of long lines : 8.41
shift : 7.15
shift of filter section : 8.10, 3.15
shift, of resistance - capacity network : 8.20
shift, video amplifiers : 7.12
shifter capacity, 3.22, 18.3
shifter continuous : 3.20
0-180° : 3.24
potentiometer : 3.23, 18.3
splitter : 7.22
velocity : 5.6, 5.8

INDEX

- Phosphorescence : 6.7, 6.9
- Pinch construction and lead inductance : 7.26
- Piston attenuator : 5.24
- Plan position indicator : 11.12
- Plates, shaped : 6.18
- Plate, splitting : 6.25
- Plan position indicator : 11.12
- Polar diagram (see field strength diagram)
- Polarisation, of electromagnetic wave : 17.3
- Polyphase rectifier circuits : 20.4
- Polyrod aerial : 17.59
- Poly-vinyl chloride : 4.45
- Post deflector acceleration : 6.24
- Positive ion bombardment : 6.37
- Potential : distribution between two cylinders : 8.25
 - distribution in diode : 15.7
 - ionisation ; 6.35
 - mean, of CRT plates : 6.20, 6.28, 6.30
 - suppressor grid : 6.34
- Potentiometer, automatic (electronic) earthing circuit : 20.17
 - 8-feed point : 3.23
 - 4-feed point : 3.23
 - inductive : 19.6
 - linearity of : 7.19
 - sine : 3.18, 3.23
 - sine-graded resistive : 19.6
 - transmission system : 19.5
- Power : amplifiers, biasing for : 7.4
 - amplifiers : 7.20
 - anode : 20.1
 - cathode heating : 20.1
 - dissipated in line load : 4.12
 - factor : 1.14
 - gain, of aerial, definition : 17.9
 - gain of cosec-mirror : 17.51
 - gain, of end-fire array : 17.39
 - gain, of halfwave aerial : 17.10
 - gain, of paraboloid : 17.19, 17.53
 - gain, of receiving aerial : 17.14, 17.15, 17.16, 17.17, 17.18
 - gain, of transmitting aerial : 17.14, 17.15, 17.16, 17.17, 17.18
 - gain, of Yagi aerial : 17.42
 - oscillators : 8.43
 - standing-wave ratio : 4.39
 - supplies, CRT : 6.26, 6.1, 6.2, 6.12, 6.14, 6.16, 6.17, 6.28
 - supplies, impedance of : 7.3
 - supplies, oscillators : 8.43, 8.44, 8.45
 - supplies, oscillators, fluctuations in : 8.43
 - supplies, screen and anode supply for frequency stabilisation : 8.43
 - supplies, screen grid : 7.5
 - supplies shift : 6.28, 6.29
 - supplies, stabilised : 6.36
 - valves : - 6.33
- RFI : 7.12
- Pre - bootstrap : 14.21
 - modulator : 14.20
- Pre single valve : 14.22
- Preplumbing, of magnetrons : 8.42
- Pressure, in CRT : 6.1, 6.2
- Pretuning, of magnetrons : 8.35
- Primary : feed : 17.49, 17.52
 - reverse and forward components : 8.31
 - sources of radiation : 17.48, 17.49, 17.52, 17.53

INDEX

Principal modes : 4.7
Propagation between parallel plates : 5.9
 constant : 4.17
 of filter sections : 3.10
 of network : 3.3
 electromagnetic wave : 4.1
 in rectangular tubes : 5.9
Protection of contactor coils : 6.44
Protection of soft rhumbatron : 6.42
 power supplies : 6.44
Protective : device for quenched oscillators : 8.47
 devices in waveguides : 5.44
Puckle time base : 11.9
Pulse, amplification of : 7.11
 design, considerations 14.15
 modulator : 14
 priming : 16.39
 relection 9.7
 RF reception of 16.1
 shape : 8.1
 shaping : 6.44
 suppression : 16.39, 16.40
 transformer : 14.12
 with delay networks : 14.19
 with hard valve modulation : 14.18
Pulse - forming network : 13.4
Pulses : coherent : 16.2, 16.3
 delay line : 13.4
 distortion, of, in receiver : 16.1, 16.3
Pulses : duration, choice of, 16.4
 high voltage : 6.33
 non-coherent : 16.2
 pulse forming, network : 13.4
 ringing circuit : 13.3
 short duration, production of 13
Push-pull : 4.38
 oscillators : - 8.19
 π - mode : 8.31, 8.35

Q

Q-factor : 7.8
 of a circuit : 1.19
 of a coil : 1.15
 of a component : 1.16
 of resonant line : 4.27
 variation of with frequency : 1.15
Q- of aerial array : 17.45
 of half wave aerial : 17.12, 17.41
 of rhumbatron 16.28
Quarter wave can : 17.43
 can, skirt or Balun : 4.38
 length line : 4.27
 matching sections : 4.34
 matching transformer : 17.44
 sleeve rejector : 4.30
 transformers : 4.29, 4.54
Quench frequency : 8.48

R

Radiation, losses, in valves : 7.24
 resistance noise, associated with : 15.4
 of aerial : 17.11, 17.13, 17.34, 17.41, 17.44
Radio-frequency amplification : 7.8
 amplifier, ideal : 3.8
 amplifier, practical : 16.9

INDEX

- Range : calibration : 18.5
 - connections : ballistic : 18.4
 - bias : 18.4
 - displacement : 18.4
 - zero error : 18.4
- Range : datum : 18.4
- Range displays : circular (Type T) : 18.3, 18.20
 - expanded : 18.21
 - flat spiral : 18.19
 - plan position indicator : 18.18
 - spiral : 18.3
 - Type A : 18.2
 - Type B : 18.18
- Range indicator : 18.1, 18.2, 18.9
 - indicated : 18.5
- Range marker : 18.1, 18.19
 - dunkelpunkt (darkspot) : 18.21
 - notch : 18.9
 - pedestal : 18.9
 - step : 18.9
 - strobe (bright spot) : 18.9
- Range : maximum, of radar set : 17.19
- Range : measurement : Chap.18
 - "decade" potentiometer rheostat : 18.15
 - exponential potentiometer : 18.14
 - exponential rheostat : 18.13
 - linear condenser : 18.11
 - linear resistance : 18.12
- Range potentiometer leakage effects : 18.16
- Range timebase : coarse 18.17
 - fine : 18.17 to 18.21
 - waveforms : exponential : 18.1, 18.2
 - linear : 18.1, 18.2
 - sawtooth : 18.2, 18.7, 18.10
 - sinusoidal : 18.1, 18.3, 18.8
- Raster : 6.17
- Ratio, damping : 1.21
- Reactance : 1.11
- Reactance curves : 1.18
- Reactances stub : 4.31
- Reaction : 8.3
- Reactors, saturable : 19.14
- Receiver, centimetre wavelengths : 16.34
 - decimetre wavelength : 16.33
 - input valves : 7.25, 7.26
 - meter wavelength : 16.33
 - radar : 16.30
 - superheterodyne : 16.1, 16.5, 16.6, 16.15, 16.30
- Receivers, differential : 19.12
 - magslip : 18.11
 - selsyn : 19.10
- Reception of RF pulses : 16.1
- Reciprocity theorem : 1.7, 17.14
- Recombination : 6.38
- Rectangular wave : 4.5
- Rectifier circuits : 20.2 et seq
 - filter circuits : 20.1, 20.5
- Rectifiers, copper oxide : 20.2
 - diode half-wave : 20.3
 - full-wave : 20.3
 - full-wave (bridge) : 20.3
 - hot-cathode mercury vapour : 20.2
 - mercury arc : 20.2
 - three-phase, full-wave : 20.4
 - three-phase half-wave : 20.4
 - three-phase half-wave double : 20.4

INDEX

- Recurrence frequency : constant : 8.47
 - squegging oscillator : 8.47
- Recurrence rate, rotary spark : 6.41
- Reduction factor, space charge : 15.7, 15.8, 15.9
- Reference vector : 1.10
- Reflected impedance : 1.20
 - wave : 4.5
- Reflection at the termination : 4.8
 - coefficient of ground : 17.21, 17.23
- Reflection, coefficient, of sea : 17.22, 17.23
 - of radio waves, by ground : 17.20, 17.21, 17.46, 17.47
 - by sea : 17.20, 17.22
 - phase change : 17.21, 17.22, 17.23, 17.24, 17.25, 17.26
 - rectangular wave : 4.8
- Reflecting screen, behind aerial : 17.32, 17.49
 - wire netting : 17.33
- Reflector : 8.23
 - parasitic : 17.43, 17.49
 - potential in AFC circuits : 8.53
- Reflex klystron : 8.23
- Refraction, of electron beam : 6.12
 - of radio waves in atmosphere : 17.28
 - super : 17.28
- Refractive index, and equipotential planes : 6.12
 - of ground : 17.21
 - of sea : 17.22
- Regeneration : 8.12
- Regulating circuits : 20.9
- Regulation voltage : 20.9
- Regulator : AC : 20.14
 - alternating voltage : 20.15, 20.16
 - transformers : 20.13
- Rejector circuit : 1.19
- Relative vector, diagram : 1.10
- Relaxation oscillators : 8.1
- Reliability (transmission system) : 18.3
- Remaining network : 1.12
- Removed network : 1.12
- Repeats round magnetron block : 8.31
- Re-radiation by obstacle : 17.18, 17.19
 - by parasitic aerial : 17.41
 - by receiving aerial : 17.14
- Resistance : 1.3
 - coil, in series LR circuit : 2.9
 - dynamic : 1.19
 - differential : 7.3
 - load : 4.8
- Resistance, spreading of crystal : 16.23
- Resistive elements : 1.3
 - losses : 4.41, 4.42
 - potentiometers : sine grade : 19.6
- Resistor, field discharge : 6.44
- Resistors : 1.3
 - non-ohmic : 6.43, 6.45
- Resolver, capacitive : 3.17, 3.20, 3.22
 - inductive : 3.17, 3.19, 3.20, 3.21
 - resistive : 3.17, 3.18, 3.20
- Resolving power of radar set : 16.1
- Resonance : 1.19
 - operation, for frequency stabilisation : 8.43
- Resonant circuit, series : 1.18
 - frequency : 1.18
 - lines : 4.26
 - lines, and stray capacitance : 7.26

INDEX

Resonators, application of : 5.32
 cavity : 5.25 et seq
 charges and currents on internal surfaces of : 5.29
 excitation of : 5.30
 field patterns in : 5.27
 Q-factor of : 5.31
 radial time base : 11.13
 rectangular pulses production of : 9.5
 rectification : 12
 reflection in waveguides : 5.45
 relaxation oscillator : 10.1
 relays : 10.1, 10.4
 resonant wavelength of : 5.28
 ring filters in waveguides : 5.49
 ringing circuit to produce short pulses : 13.3
 rotary KH transformer in a waveguide : 5.49
 wavemeter : 5.32
Response, of video amplifiers : 7.10, 7.11, 7.12
Restoration, DC : 2.4, 12.2
Rhumbatron, field distribution in : 8.22
 soft : 4.40
 soft, see soft rhumbatron
 double, Klystron : 8.23
Rieke diagram : 8.40
Ring potentiometer transmission system : 18.6
 strapping : 8.35
Ringing circuit : 8.3
 2.9, 2.10
 overdamped : 7.11
 in delay network : 2.11
Rising sun magnetron : 8.27
Rotary converter, synchronous : 19.14
Rotary spark gaps : 6.39, 6.41
Rotating joint : 4.30
 joints, effect on pulse shape : 8.1
Royal Air Force Signal Manual : 1.1

S

Safety device : 6.44
Sanatron : 10.10
Saturable reactors : 19.14, 20.15
Saturation, of receiver : 16.40
Scattering, of radio waves by obstacle : 17.18
Screen current and current feedback : 7.16
Screen grid, its equivalent in cathode ray tube : 6.12
Screen, reflecting : 17.32, 17.33
 slotted in cathode ray tube : 6.18
 supply circuit : 7.15, 8.43
Screen balanced pair : 4.38
Sea-clutter, 17.26
Second order servo, zero velocity lag : 19.22
Secondary : 1.3
Secondary emission, from anode 6.34 : (see also electrons secondary)
 from suppressor : 6.34

INDEX

- Sections matching : 4.32
 - quarter wave : 4.34
 - trombone : 4.38
- Selectivity : 7.8
 - and stray capacity : 7.26
 - of rhumbatrons : 16.28
- Self-inductors : 1.3
 - quenching : 8.47
 - screening tuned circuit : 4.28
- Selsyns : 19.5, 19.7, 19.8
- Selsyn receivers : 19.10
 - transmitters : 19.9
- Septate guide : 5.24
- Series, choke input filter : 20.6
 - feedback - : 7.4, 7.14, 7.16, 7.22, 7.23
 - networks : 1.14
 - resonant circuit : 1.18
- Servos : 8.49
 - D.C. : 19.16
 - metadyne system : 19.16
 - motors : 19.16
 - speed control system : 19.16
 - systems : 19.1, 19.13, et seq
 - systems performance of : 19.17
 - two-phase induction : 19.16
 - Ward-Leonard system : 19.16
- Shaped electrodes, spark 6.40
- Shaping pulses - 6.44, 8.1, 13.4
- Shield, CRT : 6.5
 - mumetal : 6.22
- Shift current : 6.29
 - networks : 6.26, 7.23
 - power supply : 6.28, 6.29
 - voltage : 6.28, 7.23
- Short circuits : 4.1
 - lengths of line : 4.2
- Shunt condenser, input filter : 20.7
- Side-bands : 16.2, 16.3
 - lobes, of aerial array : 17.30, 17.37, 17.42
 - lobes, of cheese aerial : 17.52
 - lobes, of paraboloidal aerial : 17.48, 17.50, 17.53
- Signal frequency stages, number of : 16.32
 - noise ratio, definition : 15.2
 - deterioration in receiver : 15.16
 - noise ratio, minimum : for A-display : 15.2, 15.16, 16.4, 16.31
 - for PPI. display : 15.16, 16.31
 - selection : 18.1, 18.6 to 18.8, 18.17
 - principle : 18.6
- Signal training manuals : 1.1
- Simple error control : 19.19
 - limitations of : 19.20
- Signed graded resistive potentiometers : 19.6
- Single-phase rectifier circuits : 20.3
 - transmission systems : 19.7
 - shunt stub : 4.54
 - stream steady state : 8.28
- Sinusoidal wave : 4.5
- Skiatron : 6.9

INDEX

- Skin current : 4.7
 - effect : 5.3
- Skirt, quarter wave : 4.38
- Sleeve rejector : quarter wave : 4.30
- Slewing : 19.21
- Slide-back : 9.3
- Slide-back bias : 7.23, 7.4
- Slope resistance - 7.3
- Slot aerial : 17.49, 17.59
- Slot in a resonant cavity : 5.30
- Slotted array : 17.55, 17.56
- Slotted screen - 6.18
- Slots, in waveguide : 17.54
 - radiation from : 17.54, 17.55, 17.56
 - series connected : 17.54
 - shunt-connected : 17.54, 17.55
- Slugs : 4.37, 4.54
- Soft rhumbatron : 4.40, 6.42
 - tubes, CRT : 6.17
 - valves : 6.35, 6.42
- Space charge barrier : 15.8, 15.9
 - distribution, in VM tubes
 - limitation : 15.7, 15.8
 - in magnetrons : 8.25, 8.27, 8.28, 8.30
 - in soft valves : 6.35
 - reduction factor : 15.7, 15.8, 15.9
- Spark gap : 4.40
 - gaps : 6.39
 - gap modulator : 4.26
- Sparking; premature : 6.40
- Spectrum amplitude of modulator wave : 16.2
 - of noise in klystron : 16.28
 - of rectangular pulses : 16.2
 - of RF parts : 16.2, 16.5
- Spectrum analyser : 8.1
 - continuous : 16.2
 - "white" : 16.2
- Speed control system : 19.16
- Spiral timebase : 11.12, 18.19
- Split-anode magnetron : 8.24, 8.26
- Splitting plate : 6.25
- Spot size, on CRT : 6.12, 6.20
- Spreading resistance of crystal : 16.23
- Squegger : 8.47
- Squegging, criterion for : 8.47
 - mechanism of : 8.47
 - oscillator with constant recurrence frequency : 8.47
- Stabilisation, of HT - see power supplies, stabilised
 - of oscillators : 8.43
 - of recurrence frequency : 8.47
- Stability, condition, oscillators : 8.47
 - of RF discharge : 6.42
 - of thermistors : 6.45
- Stabilovolt : 6.36
- Stacking, of radiating elements : 17.30
- Staggered tuning : 7.8
 - in IF amplifier : 16.35

INDEX

- Standing wave : 4.13 et seq
 - complete : 4.13
 - effect of frequency pulling : 8.40, 8.41
 - indication : 4.39
 - magnetron voltage pattern : 8.31
- Standing wave, partial : 4.13
 - ratio:17.53
 - ratio (SWR) : 4.13
 - power : 4.39
- Star - delta transformation : 1.13
 - mesh transformation, application of : 7.23
 - network : 1.13
- Static errors : 19.3
 - friction : 19.15
- Stationary waves and waveguides : 5.24
- Steady state : 4.10
 - errors : (servos) : 19.19
- Step-by-step transmission system : 19.4
- Stiction : 19.15
- Stiffness : 19.3, 19.19
- Stig control : 6.28
- Storage fields : 4.7
- Strapping : 8.34, 8.35
- Striking characteristics - (thyatron) : 6.38
 - voltage : 6.37, 6.38
- Strip strapping : 8.35
- Stubs : 4.31
- Stub, double shunt : 4.54
 - match, wide band : 4.38
 - matching : 4.36
 - matching, double : 4.36
 - Pawsey : 4.38
 - Reactances : 4.31
- Substitution theorem : 1.2
- Subtraction, by long tailed pair : 7.23
- Superposition theorem : 1.6, 4.4
- Superheterodyne : 16.1, 16.5, 16.15, 16.30
- Superregenerative receiver : 8.48
 - explanation of high-gain : 8.48
- Supplementary modes : 4.7
- Supply voltages - see power supplies
- Suppression of receiver : 16.39, 16.40
 - of surges : 6.44
 - pulse : 16.39, 16.40
- Suppressor-grid characteristics : 6.34
- Suppressors, closely wound : 6.34
- Surge impedance : 4.6
- Susceptance : 1.11
 - curves : 1.18
- Sutton tube : 8.23
- Swept gain : 16.40
- Switch, electronic : 6.42
- Switches, in waveguides : 5.44
- Switching, bridged contact : 6.44
 - circuit : 4.40
 - valve : 4.40
- Synchronised sparks : 6.41
- Synchronous data transmission : 19.2
 - rotary converter : 19.14
- Synthesis of an H-wave : 5.7

INDEX

T

- Tapered feed, of aerial array : 17.37
 - of cheese aerial : 17.52
 - of paraboloid : 17.48
- Temperature, effect on resistance : 6.45
 - effect on soft diodes : 6.37
 - thyratrons : 6.38
 - of anode block, effect on frequency : 8.41
 - of soft rhumbatron : 6.42
- Temporal gain : 16.40
- Termination, of cable by grounded grid valve : 7.20
- Tetrode action : 6.34
- Thermostat, for thyratrons : 6.38
- Thermostatic control, for crystals : 8.18
- Thermistors : 6.43, 6.45
- Thermistor, as ohmic resistor : 6.45
 - compensating : 6.45
 - stabilisers : 20.11
- Thevenin's Theorem : 1.12
- Three-phase full-wave rectifiers : 20.4
 - half-wave rectifiers : 20.4
- Three-phase half-wave double-Y rectifiers : 20.4
- Threshold voltage : 8.33
- Thyratron : 6.38
 - disadvantages : 6.38
 - thermostat for : 6.38
- Timebase : 11
 - amplitude control : 11.5
 - circular : 11.12
 - coarse : 18.17
 - discharge circuits : 11.8
 - elliptical : 11.12
 - expanded portion : 18.21
 - exponential : 18.1
 - fine : 18.17
 - flat spiral : 18.19
 - flyback : 11.2
 - J-scope : 18.20
 - linear : 18.2
 - linearity : 11.1
 - magnetic deflection : 11.11
 - Miller : 11.10
 - Puckle : 11.9
 - radial : 11.13
 - sawtooth : 18.2
 - sinusoidal : 18.3
 - spiral : 11.12
 - velocity control : 11.5
- Time constant, of cathode circuit in paralysis : 16.38
 - of series CR circuit : 2.2, 2.4
 - of series IR circuit : 2.6
 - of series parallel CR circuit : 2.5
 - s in amplifiers : 7.20, 7.11, 7.13, 7.15
 - s in cathode follower : 7.18
 - screen circuit : 7.5

INDEX

- Time delay, thermistors : 6.45
- Time standards primary : 18.1
 - secondary : 18.5
- Timing systems : 18.1
- Transconductance : 7.3 - see also mutual conductance
- Transformation, star-delta : 1.13
- Transformation, wide-band : 4.38
- Transformer, double half-wave : 4.54
 - cathode follower as : 7.19
 - to secure balanced input : 7.15
 - to secure balanced output : 7.21
 - variable ratio : 19.7
- Transformers : 1.2
 - balance-to-unbalance : 4.38
- Transformers, half-wave : 4.33, 4.54
 - impedance : 4.34
 - quarter-wave : 4.29, 4.54
 - regulated 20.13
- Transient response : 7.1
- Transient time, inductance compensated video stage : 7.12
 - in superregenerative circuit : 8.48
- Transit time : 7.24, 7.25
 - effect on oscillator : 7.25
 - input conductance due to : 15.10
 - noise due to : 15.10
 - typical values for : 7.25
- Transitron : 10.5
 - action of : 6.34, 8.11
 - as sinusoidal oscillator : 8.11
 - relaxation oscillator : 10.6
 - relay : 10.7
 - valves, suitable for : 6.34
- Transmission line : 4.2
- Transmission line, and interelectrode capacitance : 7.26
 - and valve leads : 7.26
 - electromagnetic waves on : 4.7
- Transmission lines, calculator : 4.47
 - limitations of : 4.41
 - long, effect on frequency : 8.41
 - loss-free : 4.3
- Transmission systems lamp : 19.4(i)
 - M-type : 19.4(ii)
 - performance of : 19.3
 - potentiometer and voltmeter : 19.5
 - ring potentiometer : 19.6
 - single-phase AC : 19.7
 - step-by-step : 19.4
- Transmitter valves - 6.33
- Transmitters, Selsyn : 19.9
- Transverse electric waves : 5.6
- Transverse magnetic waves : 5.6
- Trigger electrode : 6.39
- Triggered spark gap : 6.39, 6.40
- Triggering, mechanism of : 6.40
 - methods of : 6.40
- Triode, grounded-grid : 16.14, 16.34
 - input conductance of : 16.14
 - neutralised : 16.34

INDEX

Triodes, soft : 6.38
Trombone matching section : 4.38
Tunable magnetrons : 8.36
Tuned anode oscillator : 7.7, 8.12, 8.5
 circuit for oscillators : 8.17
 circuit, self-screening : 4.28
 grid oscillator : 8.4, 8.12
Tuning range, of oscillators : 8.12
Twist, coaxial : 4.2
Twisted pair : 4.2
Twists in waveguides : 5.48
Two-phase, Selsyn system : 19.8
Two-terminal networks, frequency characteristics of : 1.18

U

U-circles : 4.49
Unbalanced line : 4.38
Unbounded medium : 4.7
Undamped natural angular frequency : 19.19
 frequency : 19.18
Unit function : 19.17
Unit function response : 19.17, 19.19
Units of deflection sensitivity : 6.17
universal resonance curve : 1.18, 1.19

V

Valve, reactance effects of : 8.3
 stabilisers, hard : 20.12
 neon : 20.10
Valves, acorn : 6.33
Valves at high frequencies : 7.24, 7.26
 doorknob : 6.33, 7.25
 hard : 6.32, 6.34
 neon : 6.36
 power : 6.33
 soft : 6.35, 6.42
 stabilivolt : 6.36
 types for receiver input : 7.25, 7.26
Variable ratio transformer : 19.7
Variation of line voltage or current, experimental wave : 4.5
 rectangular wave : 4.5
 sinusoidal wave : 4.5
Vector diagrams : 1.10
 relative : 1.10
 reference : 1.10
 representation : 1.8, 4.21
Vectors, addition and subtraction of : 1.10
 E.4.3
 H.4.3

INDEX

Velocity : 4.3
lag : 19.19, 19.22
modulated amplifier : 8.22
modulated tubes : 8.21, 8.23
tubes, density modulation in : 8.22
modulation, explanation of : 8.23
inefficiency of : 8.21, 8.22
modulating tube, limitations of : 8.22
similarity to class C amplifier : 8.22
Vernier screw : 4.28
Vibrator packs : 20.1
Video amplification : 7.9
frequency stage, frequency response of : 16.5, 16.6
Viscosity : 19.15
artificial : 19.21
negative : 19.21
Viscous friction : 19.15
Voltage, and current feedback, combined : 7.17
doubler : 20.3
doubler, for cathode ray tube supply : 6.27
extinction : 6.36, 6.37, 6.38, 6.42
feedback : 7.14, 7.15, 7.22
multiplying circuits : 14.37
non-sinusoidal, application to simple circuits : 2.1
regulation : 20.9
Voltmeter transmission systems : 19.5

W

Wall currents in waveguides : 5.15
Ward-Leonard system : 19.16
Water-vapour, effect of on refraction : 17.28
for soft rhombatron : 6.42
Wave, current : 4.3
direct : 4.8
experimental : 4.5
fronts : 4.7
guide : 4.2
impedance, of free space : 17.7
length : 4.6
propagation, electromagnetic : 4.1
rectangular : 4.5
reflected : 4.5
sinusoidal : 4.5, 4.6
Waveguide feeding of aerial by : 17.49
flared : 17.52
modes, in cheese aerial : 17.52
slots in : 17.54, 17.55, 17.56
Waveguides : advantages of at cm. wavelength : 5.5
admittance of an obstacle in : 5.40
attenuating section : 5.39
attenuation coefficient : 5.5
circular : 5.17 et seq
choice of shape and dimensions : 5.33
elimination of a reflected wave : 5.42

INDEX

Waveguides : impedances : 5.36
iris : 5.43 et seq
loss coefficients in : 5.23
matching devices : 5.43
reflection from irregularity in : 5.40
reflectionless termination : 5.38
reflections from termination : 5.37
septate : 5.21
standing wave indicator : 5.41
stationary waves in : 5.26, 5.36
wavelength in : 5.6
Wavelengths in a waveguide : 5.6
Wavemeter coaxial line : 5.32
resonant cavity : 5.32
Waves : classification in circular guides : 5.19
E in circular guides : 5.20
E_{nm} in circular guides : 5.19
H in circular guides : 5.18, 5.22
H_{nm} in circular guides : 5.22
E in rectangular guides : 5.6
E_{nm} in rectangular guides : 5.16
H in rectangular guides : 5.6
H_{nm} in rectangular guides : 5.16
Attenuation in waveguides : 5.23, 5.24
Launching in waveguides : 5.14, 5.22
H wave synthesis of : 5.7
Wide-band matching device : 4.38
stub match : 4.38
stub support : 4.54
Wien bridge oscillator : 8.20
Work voltage : 5.30

Y

Yagi array : 17.42, 17.43, 17.59
Y network : 1.13

Z

Zero velocity lag, second order servo : 19.22

This file was downloaded
from the RTFM Library.
Link: www.scottbouch.com/rftm
Please see site for usage terms,
and more aircraft documents.

